

Richard Ojo

Lab 2 Report

LAB2 (a) Broken Adder Testing

```
module myAdder(A, B, CI, SUM, CO);
input CI;
input [7:0] A;
input [7:0] B;
output [7:0] SUM;
output CO;
wire [8:0] tmp;
  assign tmp = A + B + CI;
  assign SUM = tmp [7:0];
  assign CO = tmp [8];
endmodule
```

1) Broken Adder Exhaustive Testing

Testbench Code

```
module lab2atestbench();
reg [7:0] A, B; // Two Adder 8-bit inputs
wire [7:0] S, S_expected; //Adder Sum
wire Co, Co_expected;

reg [31:0] errors;

// instantiate device under test
ripple_adder dut (.X(A), .Y(B), .S(S), .Co(Co) );
myAdder expected (.A(A), .B(B), .CI(1'b0), .SUM(S_expected), .CO(Co_expected) );

integer i; //iterate for input A
integer j; //iterate for input B

initial begin
  errors = 0; // Initialize
  A = 8'h00; B = 8'h00; #10;

  for (i = 0; i <= 255; i = i + 1) begin
    for (j = 0; j <= 255; j = j + 1) begin
      // $display("Expected = %d CarryOut = %d", S_expected, Co_expected);
      // $display("RippleAdder Sum = %d CarryOut = %d", S, Co);

      if(S !== S_expected) begin
        $display("Error at time %t: A = %h B = %h got %h, expected %h", $time, A, B,
          S, S_expected);
        errors = errors + 4'b0001; #1;
      end
    end
  end
end
```

```

        B = B + 4'b0001; #10; //Push next input to adder
    end

    A = A + 4'b0001; #10; //Push next input to adder

end

$display("Tests completed with %d errors", errors);
$finish; // End simulation
end

endmodule

```

Display Output

```

# Error at time          669493: A = fe B = 21 got df, expected 1f
# Error at time          670124: A = fe B = 60 got 1e, expected 5e
# Error at time          670135: A = fe B = 61 got 1f, expected 5f
# Error at time          670766: A = fe B = a0 got 5e, expected 9e
# Error at time          670777: A = fe B = a1 got 5f, expected 9f
# Error at time          671408: A = fe B = e0 got 9e, expected de
# Error at time          671419: A = fe B = e1 got 9f, expected df
# Error at time          672060: A = ff B = 20 got df, expected 1f
# Error at time          672701: A = ff B = 60 got 1f, expected 5f
# Error at time          673342: A = ff B = a0 got 5f, expected 9f
# Error at time          673983: A = ff B = e0 got 9f, expected df
# Tests completed with      16384 errors
# ** Note: $finish      : C:/Modeltech_pe_edu_10.4a/examples/lab2atestbench(42)
#   Time: 674314 ns  Iteration: 0  Instance: /lab2atestbench
# 1
# Break in Module lab2atestbench at C:/Modeltech_pe_edu_10.4a/examples/lab2atestbench line 42
VSIM 37>

```

2) Broken Adder Randomized Testing

Test Bench Code

```

module lab2arandomtestbench();
    reg [7:0] A, B; // Two Adder 8-bit inputs
    wire [7:0] S, S_expected; //Adder Sum
    wire Co, Co_expected;
    reg [31:0] errors;

    // instantiate device under test
    ripple_adder dut (.X(A), .Y(B), .S(S), .Co(Co));
    myAdder expected (.A(A), .B(B), .CI(1'b0), .SUM(S_expected), .CO(Co_expected));

    integer seed; //8bit seed

    initial begin
        // Initialize
        A = 8'h00; B = 8'h00; #10;
        seed = 8;
    end
endmodule

```

```

errors = 0;

forever begin
    A = $random(seed); B = $random(seed); #10;

    $display("Expected = %d CarryOut = %d", S_expected, Co_expected);
    $display("RippleAdder Sum = %d CarryOut = %d", S, Co);

    if(S != S_expected) begin
        $display("Error at time %t: A = %h B = %h got %h, expected %h", $time, A, B, S, S_expected);
    end

    $stop;
    $finish; // End simulation
end

end
end
endmodule

```

Display Output

```

VSIM 22> run -all
# Expected = 133 CarryOut = 1
# RippleAdder Sum = 133 CarryOut = 1
# Expected = 238 CarryOut = 0
# RippleAdder Sum = 238 CarryOut = 0
# Expected = 18 CarryOut = 1
# RippleAdder Sum = 18 CarryOut = 1
# Expected = 251 CarryOut = 0
# RippleAdder Sum = 59 CarryOut = 1
# Error at time 71: A = 9e B = 5d got 3b, expected fb
# ** Note: $finish : C:/Modeltech_pe_edu_10.4a/examples/lab2arandomtestbench.v(25)
# Time: 72 ns Iteration: 0 Instance: /lab2arandomtestbench
# 1
# Break in Module lab2arandomtestbench at C:/Modeltech_pe_edu_10.4a/examples/lab2arandomtestbench.v line 25

```

LAB2 (b) - Broken FSM Testing

Test Bench Code

```
module lab2btestbench();
reg Clock, Reset, In;
wire Out;
wire [2:0] State;

reg [7:0] TestValues [0:23]; //Test values from file

fsmtemp dut(.Clock(Clock), .Reset(Reset), .In(In), .Out(Out), .State(State) );

integer i, j;

//generate clock
initial Clock = 0;
always begin
    Clock = ~Clock; #5; // 10ns period
end

initial begin
    $readmemb("TestValues.input", TestValues); // Read vectors into TestValues, Note: $readmemb reads
testvector files written in hexadecimal
    Reset = 1; #10; Reset = 0; #10; // Apply reset
    Reset = 1; #10; Reset = 0; #10; // Apply reset
    Reset = 1;
    $display("Initial FSM state: %h", State); //Observe initial State

    //Outer for loop iterates through each 8-bit chunk
    for (i = 0; i < 23; i = i + 1) begin
        $display("TestValues[%d] = %h or %b", i, TestValues[i], TestValues[i] );

        //Inner for loop iterates through each bit
        for (j = 0; j < 8; j = j + 1) begin
            In = TestValues[i][j]; #10; //Push input bit to fsm
        end

        $display("FSM state: %h Output: %h", State, Out); //Observe State
        Reset = 0; #10; Reset = 1; #10; // Apply reset wait
    end
end
```

```
        end
        $finish;//The end of test
    end
endmodule
```

Display

Passing input patterns will have an FSM state 4 and Output: 1*
Failing input patterns will reset to State 0*

```


VSIM 4> run -all
# ** Warning: (vsim-PLI-3407) Too many data words read c
# Time: 0 ns Iteration: 0 Instance: /lab2btestbench
# Initial FSM state: 0
# TestValues[ 0] = 00 or 00000000
# FSM state: 0 Output: 0
# TestValues[ 1] = ff or 11111111
# FSM state: 0 Output: 0
# TestValues[ 2] = ab or 10101011
# FSM state: 3 Output: 0
# TestValues[ 3] = b6 or 10110110
# FSM state: 3 Output: 0
# TestValues[ 4] = b0 or 10110000
# FSM state: 1 Output: 0
# TestValues[ 5] = 58 or 01011000
# FSM state: 2 Output: 0
# TestValues[ 6] = 2c or 00101100
# FSM state: 0 Output: 0
# TestValues[ 7] = 16 or 00010110
# FSM state: 0 Output: 0
# TestValues[ 8] = 0b or 00001011
# FSM state: 0 Output: 0
# TestValues[ 9] = 55 or 01010101
# FSM state: 2 Output: 0
# TestValues[10] = aa or 10101010
# FSM state: 3 Output: 0
# TestValues[11] = d0 or 11010000
# FSM state: 4 Output: 1
# TestValues[12] = d1 or 11010001
# FSM state: 4 Output: 1
# TestValues[13] = d2 or 11010010
# FSM state: 4 Output: 1
# TestValues[14] = d4 or 11010100
# FSM state: 4 Output: 1
# TestValues[15] = d8 or 11011000
# FSM state: 0 Output: 0
# TestValues[16] = d3 or 11010011
# FSM state: 4 Output: 1
# TestValues[17] = d6 or 11010110
# FSM state: 0 Output: 0
# TestValues[18] = dc or 11011100
# FSM state: 4 Output: 1
# TestValues[19] = d7 or 11010111
# FSM state: 4 Output: 1
# TestValues[20] = de or 11011110
# FSM state: 0 Output: 0
# TestValues[21] = df or 11011111
# FSM state: 0 Output: 0
# TestValues[22] = c0 or 11000000
# FSM state: 0 Output: 0
# ** Note: $finish : C:/Modeltech_pe_edu_10.4a/examples/lab2btestbench.v(38)
# Time: 2340 ns Iteration: 0 Instance: /lab2btestbench
# 1
# Break in Module lab2btestbench at C:/Modeltech_pe_edu_10.4a/examples/lab2btestbench.v line 38
VSIM 5> quit -sim

```

Waveform

Passing input patterns will have a State: 3'h4 and Out: 1*

 Failing input patterns reset to State: 3'h0 and Out: 0*



It appears that passing input patterns begin with 1101.